
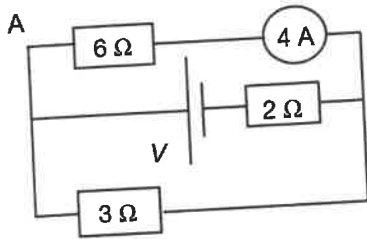


3.5.8 Analysing circuits with series and parallel resistors.

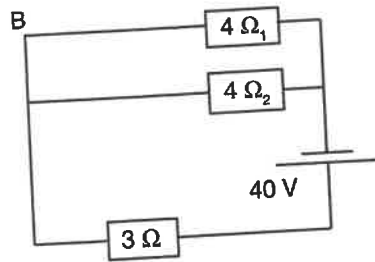
3.5.8.1 Analyse each of the following circuits to determine values for the quantities indicated.




- A**
- Total resistance =
 - Circuit current =
 - Current through 6Ω =
 - Current through 2Ω =
 - Current through 3Ω =
 - Potential across 6Ω =
 - Potential across 2Ω =
 - Potential across 3Ω =
 - Potential of source =



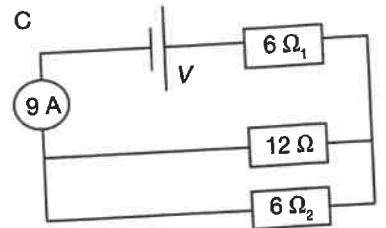
- B**
- Total resistance =
 - Circuit current =
 - Current through 3Ω =
 - Current through $4 \Omega_1$ =
 - Current through $4 \Omega_2$ =
 - Potential across 3Ω =
 - Potential across $4 \Omega_1$ =
 - Potential across $4 \Omega_2$ =



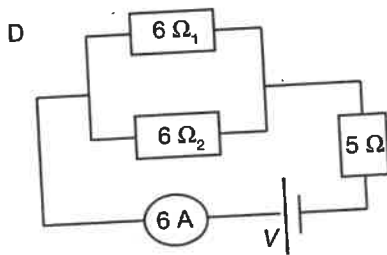
- C**
- Total resistance =
 - Circuit current =
 - Current through $6 \Omega_1$ =
 - Current through 12Ω =
 - Current through $6 \Omega_2$ =
 - Potential across $6 \Omega_1$ =
 - Potential across 12Ω =
 - Potential across $6 \Omega_2$ =
 - Potential of source =



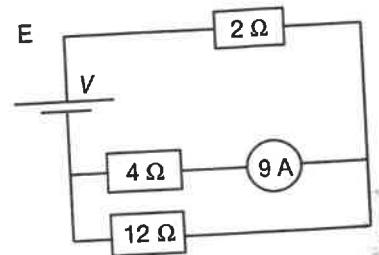- D**
- Total resistance =
 - Circuit current =
 - Current through $6 \Omega_1$ =
 - Current through $6 \Omega_2$ =
 - Current through 5Ω =
 - Potential across $6 \Omega_1$ =
 - Potential across $6 \Omega_2$ =
 - Potential across 5Ω =
 - Potential of source =




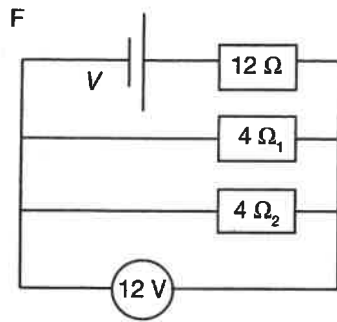- E**
- Total resistance =
 - Circuit current =
 - Current through 2Ω =
 - Current through 4Ω =
 - Current through 12Ω =
 - Potential across 2Ω =
 - Potential across 4Ω =
 - Potential across 12Ω =
 - Potential of source =




F

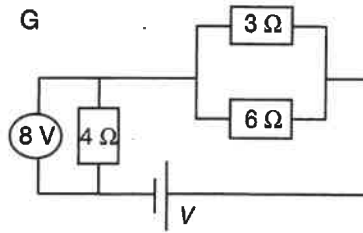- Total resistance =
 Circuit current =
 Current through $12\ \Omega$ =
 Current through $4\ \Omega_1$ =
 Current through $4\ \Omega_2$ =
 Potential across $12\ \Omega$ =
 Potential across $4\ \Omega_1$ =
 Potential across $4\ \Omega_2$ =
 Potential of source =




G

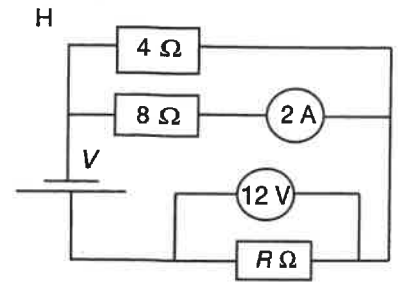- Total resistance =
 Circuit current =
 Current through $3\ \Omega$ =
 Current through $6\ \Omega$ =
 Current through $4\ \Omega$ =
 Potential across $3\ \Omega$ =
 Potential across $6\ \Omega$ =
 Potential across $4\ \Omega$ =
 Potential of source =




H

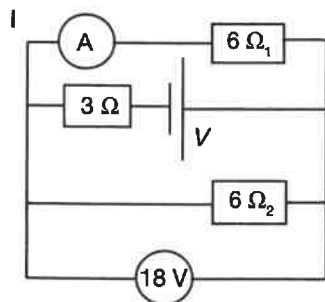- Total resistance =
 Circuit current =
 Current through $4\ \Omega$ =
 Current through $8\ \Omega$ =
 Current through $R\ \Omega$ =
 Potential across $4\ \Omega$ =
 Potential across $8\ \Omega$ =
 Potential across $R\ \Omega$ =
 Potential of source =
 Value of resistor R =



I

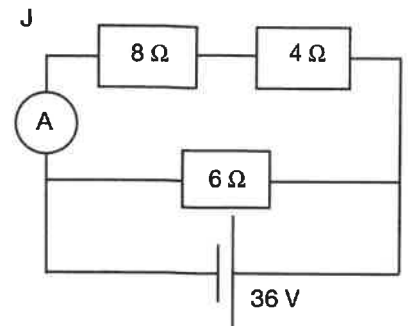- Total resistance =
 Circuit current =
 Current through $6\ \Omega_1$ =
 Current through $6\ \Omega_2$ =
 Current through $3\ \Omega$ =
 Potential across $6\ \Omega_1$ =
 Potential across $6\ \Omega_2$ =
 Potential across $3\ \Omega$ =
 Potential of source =
 Reading on meter A =



J

- Total resistance =
 Circuit current =
 Current through $8\ \Omega$ =
 Current through $4\ \Omega$ =
 Current through $6\ \Omega$ =
 Potential across $8\ \Omega$ =
 Potential across $4\ \Omega$ =
 Potential across $6\ \Omega$ =
 Potential of source =
 Reading on meter A =