

Physics 2AB

Electrical Physics Unit Test 2016

Name:

Mark: / 61

= %

Time Allowed: 50 minutes

Notes to Students:

- You must include **all** working to be awarded full marks for a question.
- Marks will be deducted for incorrect or absent units and answers stated to an incorrect number of significant figures.
- **No** graphics calculators are permitted – scientific calculators only.

Question 1**(10 marks)**

A calculator has a rated operating current of 5.00 mA and a voltage of 1.50 V

- (a) Calculate the number of electrons that flow through a point in the calculator every minute.

(4 marks)

- (b) The battery in the calculator can supply a constant charge of 4.86×10^3 C at the rated current. Calculate the operating time, in hours, the calculator can be used for.

(3 marks)

- (c) Calculate the amount of energy each electron transfers as it passes through the calculator.

(3 marks)

Question 2**(9 marks)**

An air-conditioning unit of a house has a power rating of 2.50 kW at 240 V. It is turned on in the middle of summer at 3:00 pm and runs continuously until 10:00 pm. The cost of electricity at this time is 28.0 cents per kWh.

- (a) Calculate the amount of energy, in MJ, the air-conditioner uses in this time period.

(3 marks)

- (b) Calculate the cost of running the air-conditioner for this time period.


(3 marks)

- (c) The air-conditioner has a 'power saving mode' which reduces the power rating to 1.60 kW at 240 V. Calculate how much money would be saved in this time period if the power saving mode was used.

(3 marks)

Question 3**(8 marks)**

Consider the following circuit:

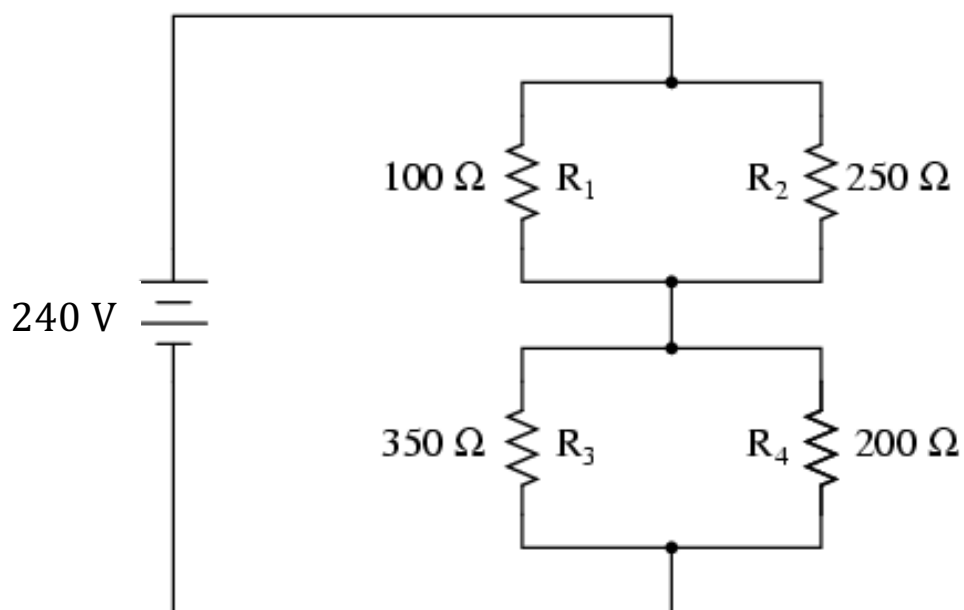

- (a) Calculate the total resistance of the circuit.

[3 marks]

- (b) Calculate the current that flows through R_1 .

[3 marks]

(c) Calculate the voltage across R_4


[2 marks]

Question 4

(6 marks)


There are many safety features incorporated into household electrical circuits to protect the occupants of the house. Explain how the following safety features operate.

a) Feature 1: Earth Wire

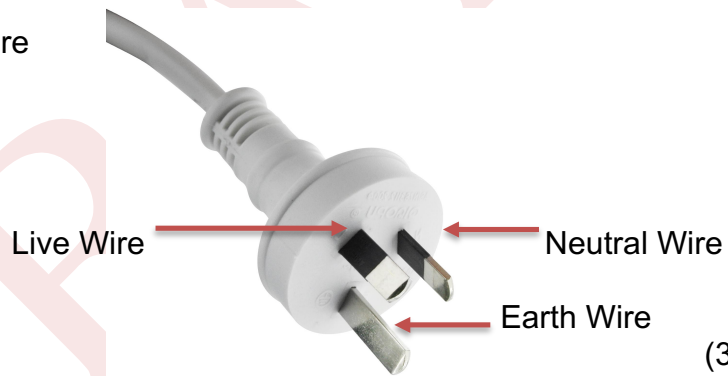

(3 marks)

b) Feature 2: Fuse

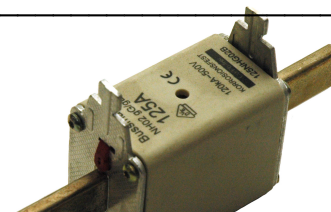

(3 marks)

Question 5

(5 marks)


A student wishes to determine the electrical resistivity of a steel rod. The length is measured as 43.5 cm and the diameter is measured as 1.80 cm. The student places the rod in a circuit and measures the voltage across the rod as 4.50 V and the current passing through the rod as 2.20 Amps

Calculate the resistivity of the steel used to manufacture the rod.

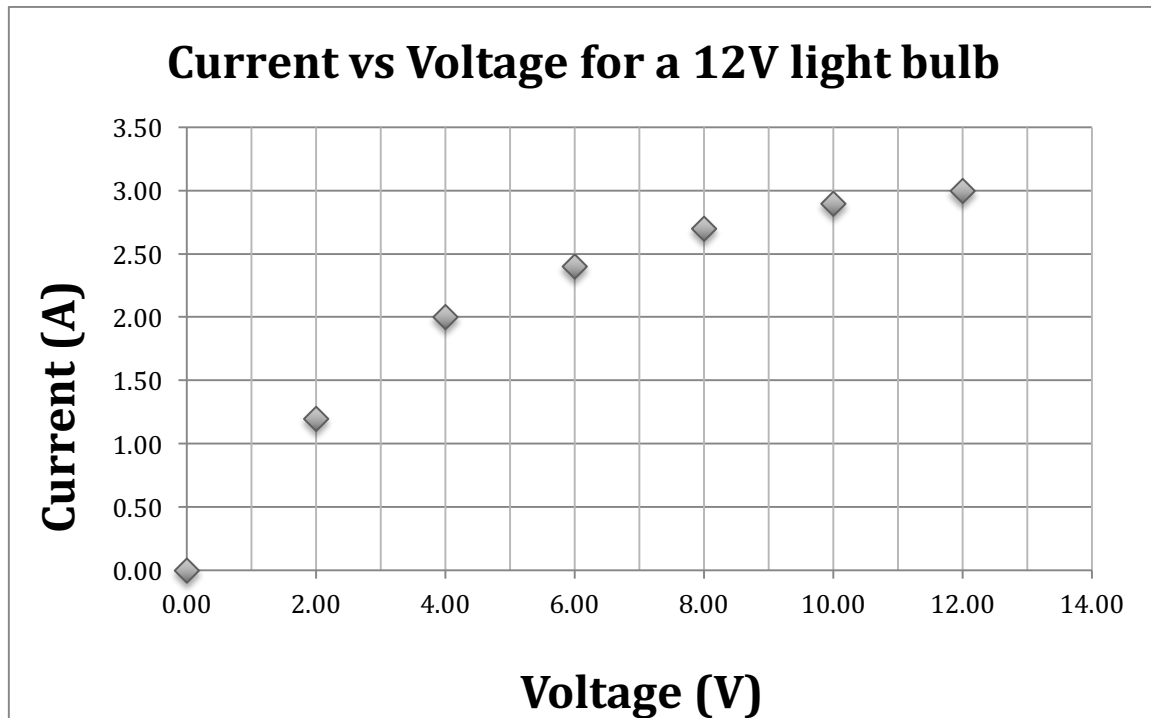Question 6

(7 marks)

A student varies the potential difference across a lamp bulb and records the current running through it. On the side of the lamp bulb is stamped the intended operating values of '12.0 V, 3.00 A'. The student produces the following graph below:



- (a) Calculate the resistance of the light bulb at the intended operating voltage of 12.0 V. (2 marks)

- (b) State if the light bulb ohmic or non-ohmic. Provide an explanation for your answer. (2 marks)

- (c) A student then obtains a 6.00 Ω resistor and varies the voltage from 0.00 to 12.0 V. Sketch the I-V Characteristic curve for the resistor on the graph above for this voltage range. Include any calculations you require in the space below. (3 marks)

Question 7


(7 marks)

A student has a $10.0\ \Omega$ electrical component that requires a voltage of $12.0\ \text{V}$. He has two $6.00\ \text{V}$ cells and two $12.0\ \text{V}$ cells.

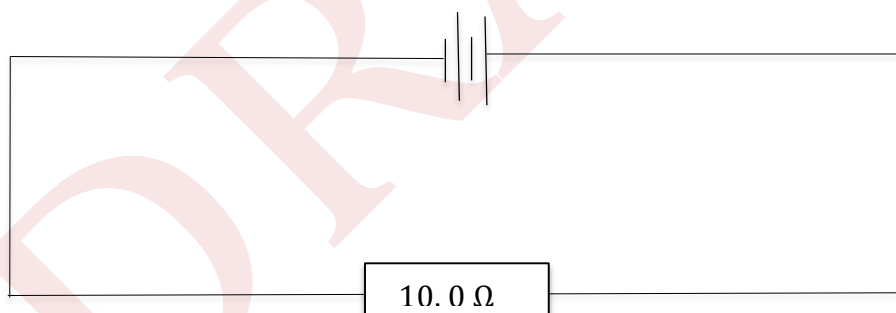- (a) Draw two circuit diagrams showing the different ways the student could arrange **only two** cells in a circuit in order for the electrical component to operate at $12.0\ \text{V}$

(4 marks)

The student places a $6.00\ \text{V}$ cell in series with a $12.0\ \text{V}$ cell in a circuit as shown in the diagram below.




- (b) Determine the current that would flow through both of the cells in this arrangement.

(3 marks)

Question 8

(9 marks)

Consider the complex circuit below.

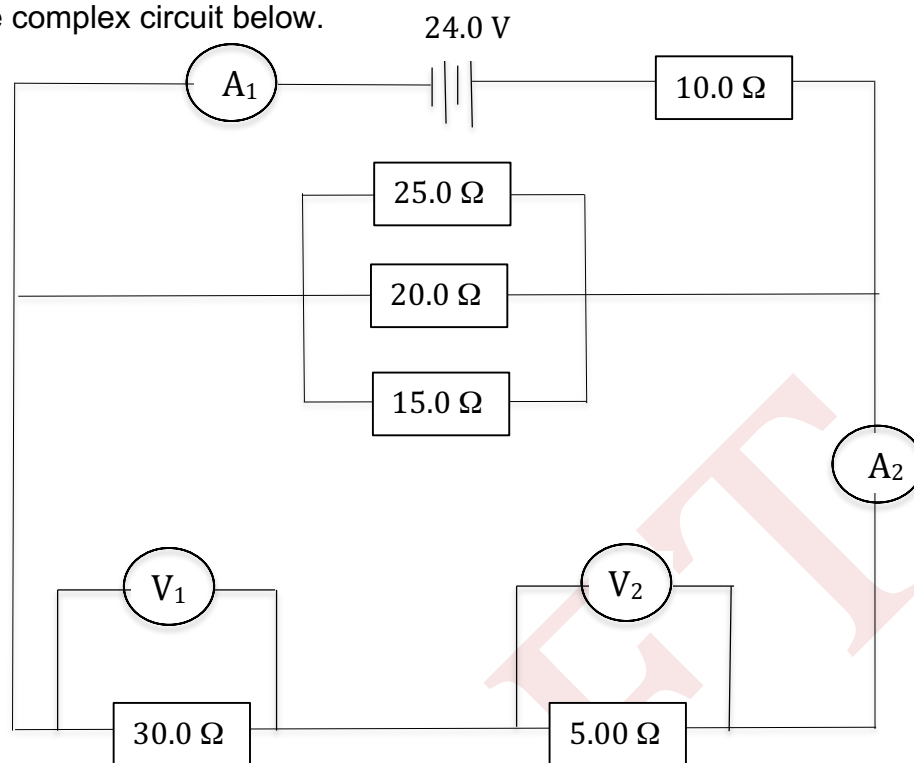

- (a) Calculate the total resistance of the circuit. (4 marks)

- (b) Calculate the total current the flows in the circuit. (2 marks)

- (c) Determine the current that flows through A_2 (3 marks)