

Physics ATAR - Year 11

Electrical Physics Unit Test 2017

Mark:	/ 63
=	%

Name:

Time Allowed: 50 minutes

Notes to Students:

- You must include **all** working to be awarded full marks for a question.
- Marks will be deducted for incorrect or absent units and answers stated to an incorrect number of significant figures.
- **No** graphics calculators are permitted – scientific calculators only.

Question 1**(7 marks)**

During a laboratory practical session, James connects a simple light circuit to a 12.0 V DC power supply.

- (a) Calculate the work done in Joules as one electron travels around the circuit.
(2 marks)
- (b) Calculate the charge that passes through the circuit in 2.00 minutes if the current through the circuit is 0.500 A.
(3 marks)
- (c) Calculate the number of electrons that are required to pass through the circuit to produce the charge in (b).
(2 marks)

Question 2**(8 marks)**

A car battery supplies a voltage of 12.6 V. It is connected in parallel to the dashboard lights (which have a total resistance of 7.12 k Ω) and the headlights (which have a total resistance of 6.00 Ω).

- (a) Draw a simple circuit diagram to represent this arrangement.
(2 marks)

(b) Calculate the potential difference across and current through the headlight bulbs.
(3 marks)

(c) Determine the power of the **dashboard** lights.
(3 marks)

Question 3 (6 marks)


Tungsten filament light globes are classified as non-ohmic devices.

(a) With the aid of two graphs, describe the differences between the current, voltage and resistance characteristics of ohmic and non-ohmic devices.
(3 marks)

(b) Older tungsten filament light globes often fail just as they are turned on, explain why this is so.
(3 marks)

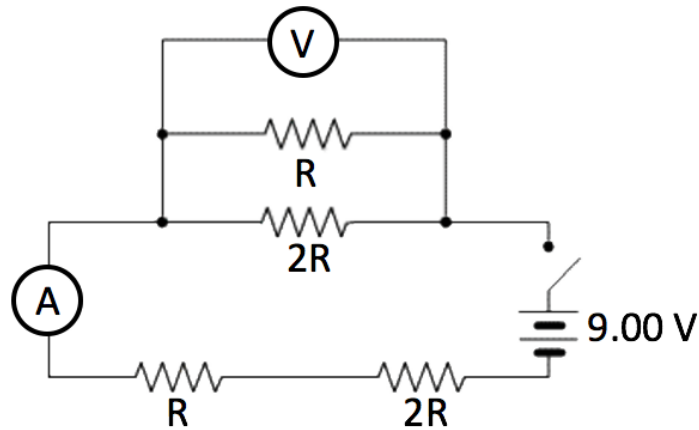Question 4**(7 marks)**

The following questions refer to the below circuit diagram, where 'R' represents a resistor of resistance ' $R \Omega$ '. Leave all your responses in terms of 'R' if applicable. You may leave your answer as a fraction or decimal.



- (a) When the switch is closed, calculate the current displayed by ammeter A. (5 marks)

- (b) When the switch is closed, calculate the voltage displayed on Voltmeter V. (2 marks)

Question 5**(10 marks)**

An electric heater is constructed by applying a potential difference of $1.20 \times 10^2 \text{ V}$ to a Nichrome wire that has a total resistance of $8.00 \ \Omega$.

- (a) Determine the current carried by the wire. (2 marks)
- (b) Determine the power rating of the heater. (2 marks)
- (c) If the heater is used for 3.00 hours each night for a week and the consumer pays 15.0 c per kilowatt hour for energy purchased, determine the cost of running the heater over one week. (3 marks)
- (d) A different Nichrome wire has a diameter of 1.30 mm. Calculate the length of wire needed to obtain a resistance of $4.00 \ \Omega$. ($\rho_{\text{Nichrome}} = 1.50 \times 10^{-6} \ \Omega\text{m}$, $R = \frac{\rho L}{A}$) (3 marks)

Question 6**(10 marks)**

While investigating an electricity failure in a workshop it becomes apparent that a fuse has melted within the main electrical panel, leaving an open circuit and preventing charge from flowing. In order to restore the electricity, an operator places a small piece of iron between the two open terminals in order to allow the flow of charge. This enables the workshop to keep operating as per normal.

- (a) Explain why this was not an appropriate fix for this problem and justify your response. (4 marks)


- (b) Fuses are being phased out of household use. Name an alternative common safety device that performs the same function as a fuse and describe how it functions. (3 marks)

During a storm, the workshop can sometimes become flooded. This creates an additional hazard due to water potentially coming into contact with live wires.

- (c) Explain why water is considered an electrical hazard. (3 marks)

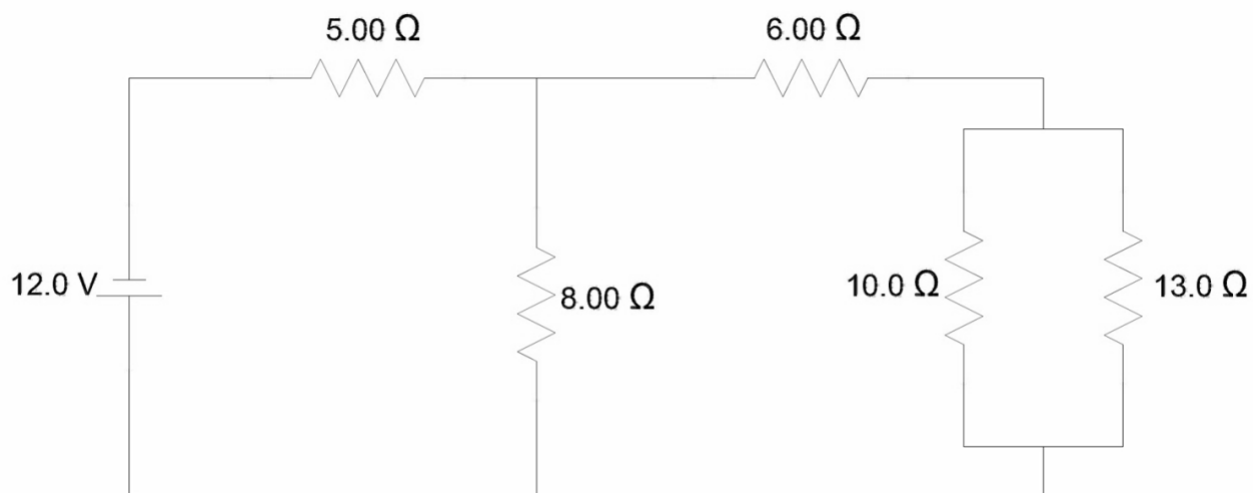Question 7**(15 marks)**

Refer to the circuit diagram below. Note you must show full and clear working to receive full marks.



- (a) Calculate the total resistance of the circuit.

(6 marks)

- (b) Calculate the total current flowing through the battery. (2 marks)
- (c) Calculate the voltage across the $5.00\ \Omega$ and the $8.00\ \Omega$ resistor. (3 marks)
- (d) Calculate the current through the $10.0\ \Omega$ resistor. (4 marks)

END OF TEST